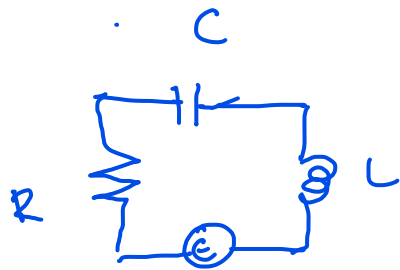


03.03.2022.

Electric circuits.



Let a source of emf be connected in series with a capacitor, a coil and a resistor as shown in figure.

I — current

By Ohm's law, the voltage drop across ^{the} resistance R is IR .

By the Law of Faraday, the voltage drop across the inductance L is $L \frac{dI}{dt}$.

If V is the voltage across the capacitor and $E(t)$ is the voltage across the source, then the voltage eqn is

$$L \frac{dI}{dt} + RI + V = E(t) \quad \text{--- (i)}$$

If C is the capacitance, it is known that the charge Q on a capacitor plate satisfies the relation $Q = CV$ (or) $\frac{Q}{C} = V$.

$$(i) \rightarrow L \frac{dI}{dt} + RI + \frac{Q}{C} = E(t) \quad \text{--- (ii)}$$

But by definition $I = \frac{dQ}{dt}$

$$\therefore L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = E(t) \quad \checkmark$$

If $E(t)=0$, electrical vibrations of the circuit are free.

Auxiliary eqn: is $Lm^2 + Rm + \frac{1}{C} = 0$

$$m = \frac{-R \pm \sqrt{R^2 - 4L/C}}{2L}$$

(i) Over damped if $R^2 - \frac{4L}{C} > 0$

(ii) Critically damped if $R^2 - \frac{4L}{C} = 0$

(iii) under damped if $R^2 - \frac{4L}{C} < 0$.

1. Find the charge $q(t)$ on the capacitor in an LCR circuit when $L = 0.25$ henry (h), $R = 10$ ohms (Ω), $C = 0.001$ Farad, $E(t) = 0$, $q(0) = q_0$ Coulombs (C), $i(0) = 0$.

$$C = 0.001 \Rightarrow \frac{1}{C} = 1000$$

$$\text{Eqn: } \frac{1}{4} q'' + 10q' + 1000q = 0 \Rightarrow q'' + 40q' + 4000q = 0.$$

$$m^2 + 40m + 4000 = 0 \quad m = -20 \pm 60i$$

$$q = e^{-20t} (c_1 \cos 60t + c_2 \sin 60t). \quad \text{--- (1)}$$

When $t=0$, $q = q_0$ Sub

$$q_0 = e^0 (c_1 \cos 0 + c_2 \sin 0) \Rightarrow c_1 = q_0.$$

$$i = 0 \text{ when } t=0 \quad (\text{i.e.}) \frac{dq}{dt} = 0 \text{ when } t=0.$$

Diff
(i).

$$\frac{dq}{dt} = e^{-20t} (-60C_1 \sin 60t + 60C_2 \cos 60t) + (C_1 \cos 60t + C_2 \sin 60t) (-20e^{-20t}).$$

$$\begin{matrix} i(0)=0 \\ i(t)=q/t=0 \end{matrix} \left| \begin{matrix} \left(\frac{dq}{dt} \right)_{t=0} = 0. \\ \hline \end{matrix} \right.$$

$$0 = 1(60)C_2 + C_1(-20)(1).$$

$$\Rightarrow +20C_1 = 60C_2 \Rightarrow 20q_0 = 60C_2 \Rightarrow C_2 = \frac{1}{3}q_0$$

$$\begin{aligned} \therefore q(t) &= e^{-20t} \left(q_0 \cos 60t + \frac{1}{3}q_0 \sin 60t \right) \\ &= q_0 e^{-20t} \left(\cos 60t + \frac{1}{3} \sin 60t \right). \end{aligned}$$

